Designing a Divider

With contributions from J. Kubiatowicz (CS152)




Divide: Paper & Pencil

See how big a number can be subtracted, creating quotient bit on each step

Binary => 1 * divisor or 0 * divisor

```
Dividend = Quotient x Divisor + Remainder
=> | Dividend | = | Quotient | + | Divisor |
```

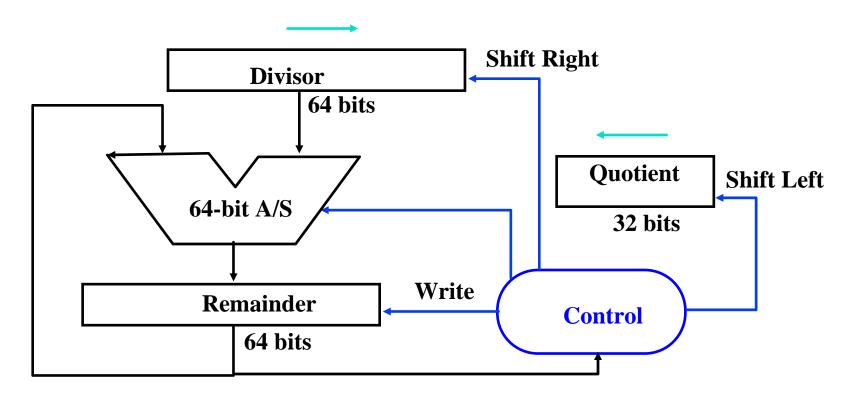64-bit Divisor reg, 64-bit ALU, 64-bit Remainder reg,
32-bit Quotient reg



Divide Algorithm Version 1

Start: Place Dividend in Remainder

°Takes n+1 steps for n-bit Quotient & Rem.

Remainder Quotient Divisor 0000 0111 0000 0010 0000

1. Subtract the Divisor register from the Remainder register, and place the result in the Remainder register.

Remainder ≥ 0

Test Remainder < 0
Remainder

2a. Shift the Quotient register to the left setting the new rightmost bit to 1.

2b. Restore the original value by adding the Divisor register to the Remainder register, & place the sum in the Remainder register. Also shift the Quotient register to the left, setting the new least significant bit to 0.

3. Shift the Divisor register right1 bit.

n+1 repetition2 No: < n+1 repetitions

Yes: n+1 repetitions (n = 4 here)

Done

igital Integrated Circuits 2/e

Divide Algorithm I example (7 / 2)

```
Remainder
               Ouotient
                          Divisor
   0000 0111
               00000
                        0010 0000
1: 1110
               00000
                        0010
                              0000
         0111
2:
         0111
               00000
                        0010
                              0000
   0000
   0000
         0111
               00000
                        0001
                              0000
         0111
               00000
                        0001
                              0000
1: 1111
                                        Answer:
2:
                              0000
   0000
         0111
               00000
                        0001
                                         Quotient = 3
   0000
         0111
               00000
                        0000
                              1000
                                         Remainder = 1
         1111
               00000
                        0000
                              1000
1: 1111
         0111
               00000
                        0000
                              1000
   0000
   0000
         0111
               00000
                        0000
                              0100
         0011
               00000
                        0000
                              0100
   0000
   0000
         0011
               00001
                        0000
                              0100
3:
   0000
         0011
               00001
                        0000
                              0010
1:
   0000
         0001
               00001
                        0000
                              0010
         0001
                              0010
   0000
               00011
                        0000
   0000
         0001
               00011
                        0000
                              0001
```

Observations on Divide Version 1


- 1/2 bits in divisor always 0
 => 1/2 of 64-bit adder is wasted
 => 1/2 of divisor is wasted
- ° Instead of shifting divisor to right, shift remainder to left?


Divide Algorithm I example: wasted space

```
Ouotient
                          Divisor
    Remainder
   0000 0111
               00000
                        0010
                             0000
1: 1110
        0111
               00000
                        0010
                             0000
   0000
        0111
                        0010
                             0000
               00000
   0000
        0111
               00000
                        0001
                             0000
        0111
               00000
                        0001
                             0000
  1111
   0000
        0111
               00000
                        0001
                             0000
   0000
        0111
               00000
                        0000
                             1000
1: 1111
               00000
                        0000
                             1000
        1111
        0111
                        0000
                             1000
   0000
               00000
   0000
        0111
               00000
                        0000
                             0100
        0011
                             0100
   0000
               00000
                        0000
   0000
         0011
               00001
                        0000
                             0100
3:
   0000
        0011
               00001
                        0000
                             0010
   0000
         0001
               00001
                        0000
                             0010
         0001
                             0010
   0000
               00011
                        0000
   0000
         0001
               00011
                        0000
                             0010
```

DIVIDE HARDWARE Version 2

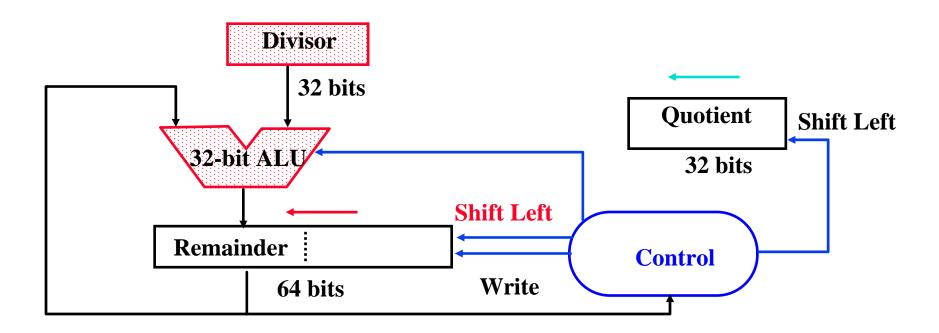° 32-bit Divisor reg, 32-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg



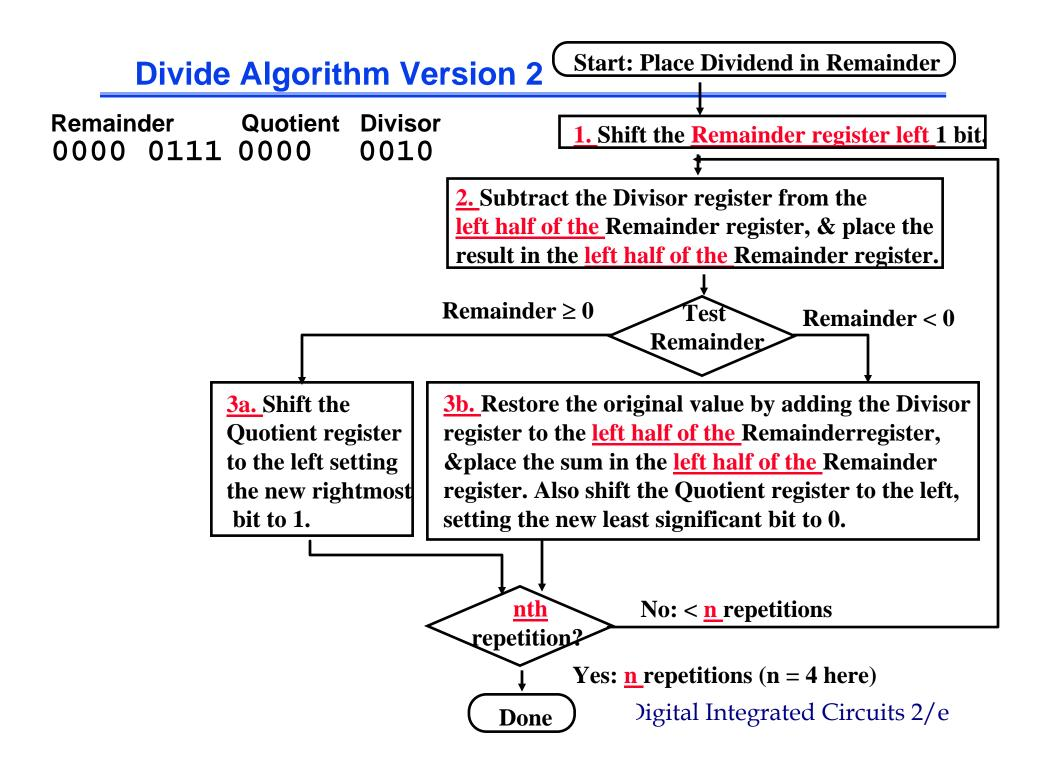


Divide Algorithm I version 2 (shift remainder)

Remainder		Quotient	Divisor
0000	0111	00000	0010
1110	0111	00000	0010
0000	0111	00000	0010
0000	1110	00000	0010
1110	1110	00000	0010
0000	1110	00000	0010
0001	1100	00000	0010
1111	1100	00000	0010
0001	1100	00000	0010
0011	1000	00000	0010
0001	1000	00001	0010
0001	1000	00001	0010
0011	0000	00001	0010
0001	0000	00011	0010
0001	0000	00011	0010
	0000 1110 0000 0000 1110 0001 1111 0001 0011 0001 0001 0001	0000 0111 1110 0111 0000 0111 0000 1110 1110 1110 0000 1110 0001 1100 0001 1100 0001 1000 0001 1000 0001 1000 0001 0000 0001 0000	0000 0111 00000 1110 0111 00000 0000 0111 00000 0000 1110 00000 1110 1110 00000 0001 1100 00000 0001 1000 00001 0001 1000 00001 0011 0000 00001 0011 0000 00001 0001 0000 00001 0001 0000 00001

Divide: Revisited

Non-restoring divider

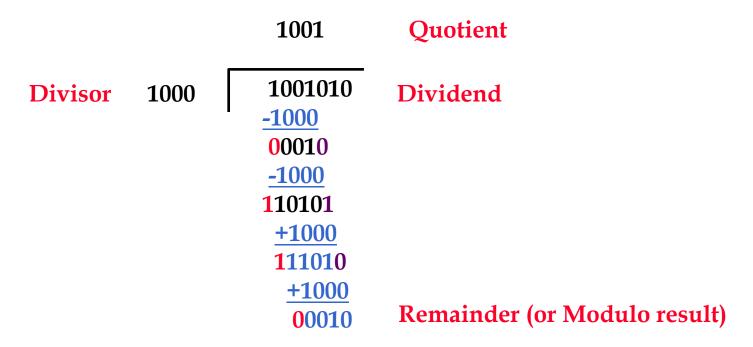

Avoids extra step of "restoration" when partial result is negative. Instead of subtract, adds divisor on next iteration

Divide Algorithm I example: non-restoring

	Remainder		Quotient	Divisor
	0000	0111	00000	0010
1:	1110	0111	0000	0010
2:	1100	1110	0000	0010
1:	1110	1110	00000	0010
2:	1101	1100	00000	0010
1:	1111	1100	00000	0010
2:	1111	1000	00000	0010
1:	0001	1000	00001	0010
2:	0011	0000	00001	0010
1:	0001	0000	00011	0010